

ASSIGNMENT-I

B-EEE


NAME :- Naveen
Kumar. S

CLASS :- CSE-B


Roll No:- 202201100

1) In the figure shown a Combination resistance, If the voltage across A & B is 75 volts. Determine.

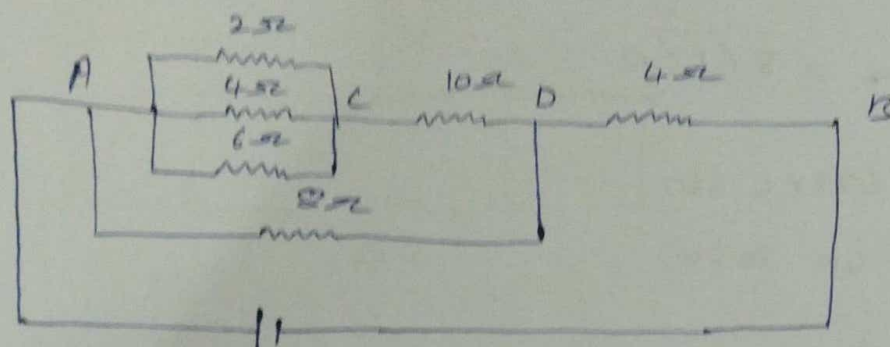- (i) The equivalent resistance of the circuit
- (ii) voltage drop across each resistance




Sol:

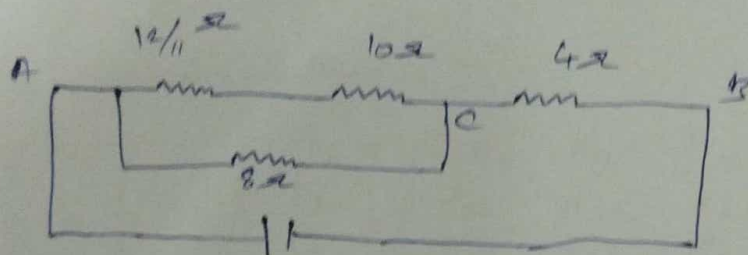


$$\frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{6}$$

$$= \frac{11}{12}$$

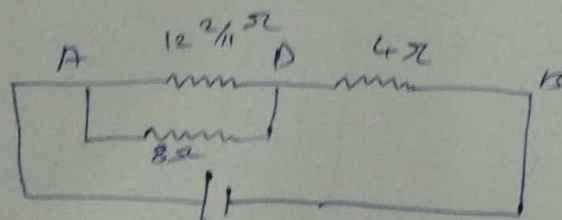


$$R = \frac{12}{11} + 10$$

$$R = \frac{122}{11}$$

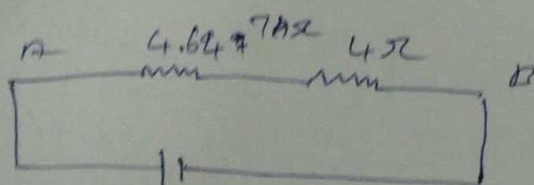

$$\frac{1}{R} = \frac{11}{122} + \frac{1}{4}$$

$$\frac{1}{R} = \frac{210}{976}$$

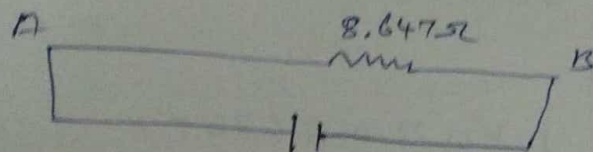

∴ The Equivalent resistance across the circuit is 8.647 Ω

$$(ii) V = 75V$$

$$R = 8.647 \Omega$$

$$I = \frac{V}{R} = \frac{75}{8.647} = 8.673 A$$

$$\therefore I_{8.647 \Omega} = 8.673 A$$

$$I_{4.647 \Omega} = I_{4 \Omega} = 8.673 A$$

$$V_{4.647 \Omega} = 8.673 \times 4.647$$

$$\therefore V_{4.647 \Omega} = 40.303 V$$

$$V_{4 \Omega} = 8.673 \times 4$$

$$V_{4 \Omega} = 34.692 V$$

$$I_{\frac{122}{11} \Omega} = \frac{8.673 \times 8}{8 + \frac{122}{11}}$$

$$\therefore I_{\frac{122}{11} \Omega} = 3.634 A$$

$$\begin{aligned} V_{\frac{122}{11} \Omega} &= 3.634 \times \frac{122}{11} \\ &= 40.8304 V \end{aligned}$$

$$I_{8 \Omega} = \frac{8.673 \times \frac{122}{11} \times 11}{88 + 122}$$

$$\therefore I_{8 \Omega} = 5.038 A$$

$$V_{8 \Omega} = 5.038 \times 8 \Rightarrow 40.304 V$$

$$I_{\frac{12}{11} \Omega} = I_{10 \Omega} = 3.634 A$$

$$V_{\frac{12}{11} \Omega} = 3.634 \times \frac{12}{11}$$

$$V_{\frac{12}{11} \Omega} = 3.964 V$$

$$V_{10 \Omega} = 3.634 \times 10$$

$$V_{10 \Omega} = 36.34 V$$

$$I_{2 \Omega} = \frac{4}{2 + 4 + \frac{2 \times 4}{6}} \times 3.634$$


$$\therefore I_{2 \Omega} = 1.982 A$$

$$\therefore V_{2 \Omega} = 1.982 \times 2$$

$$V_{2 \Omega} = 3.964 V$$

$$\therefore V_{2 \Omega} = V_{4 \Omega} = V_{6 \Omega} = 3.964 V (\because \text{Parallel})$$

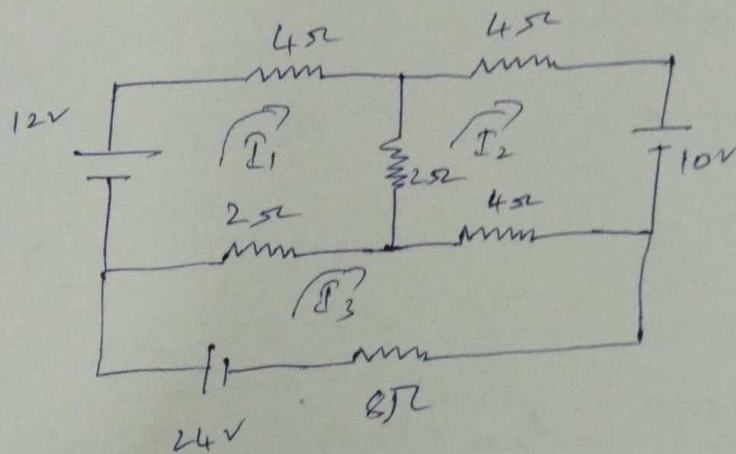7. Determine the current in each resistors in the circuit shown in figure.



Sol:

$$V = IR$$

By Inspection method:

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix}$$

$$\begin{bmatrix} 12 \\ -10 \\ 24 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 30 & -24 & -2 \\ -24 & 32 & -4 \\ -2 & -4 & 14 \end{bmatrix}$$

$$\Delta = 4,384$$

$$\Delta_1 = \begin{vmatrix} 12 & -24 & -2 \\ -10 & 32 & -4 \\ 24 & -4 & 14 \end{vmatrix} = 12(32 \cdot 14 - 16) + 24(-140 + 24 \cdot 4) + 2(40 - 24 \cdot 32) = 5584$$

$$\Delta_2 = \begin{vmatrix} 30 & 12 & -2 \\ -24 & -10 & -4 \\ -2 & 24 & 14 \end{vmatrix} = 30(-140 + 4 \cdot 24) - 12(-24 \cdot 14 - 8) - 2(-24 \cdot 24 - 10 \cdot 2) = 4000$$

$$\Delta_3 = \begin{vmatrix} 30 & -24 & 12 \\ -24 & 32 & -10 \\ -2 & -4 & 24 \end{vmatrix} = 30(32 \cdot 24 - 40) + 24(-24 \cdot 24 - 10 \cdot 2) + 12(24 \cdot 4 + 2 \cdot 32) = 9456$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{5584}{4384} = 1.273 A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{4000}{4384} = 0.912 A$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{9456}{4384} = 2.156 A$$

loop 1

$$I_{4\Omega} = 1.273 A$$

$$I_{24\Omega} = I_1 - I_2 = 0.361 A ; I_{2\Omega} = I_1 - I_2 = -0.883 A$$


loop 2

$$I_{4\Omega} = 0.912 A ; I_{4\Omega} = -1.244$$

loop 3

$$I_{8\Omega} = 2.156 A$$

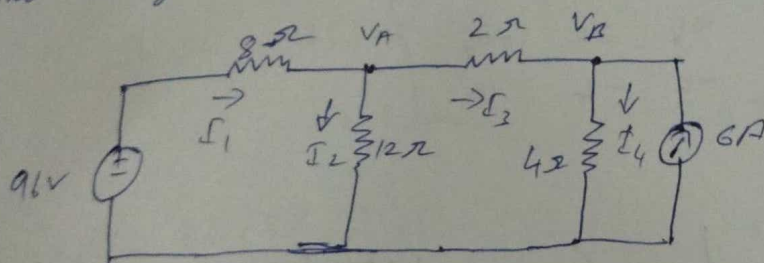3) Find voltage across 5Ω Resistor using Nodal analysis



Sol.

At Node A: By KCL

$$I_1 = I_2 + I_3$$

$$\frac{96 - V_A}{8} = \frac{V_A}{12} + \frac{V_A - V_B}{2}$$

$$(12) \quad \frac{96 - V_A}{4} = \frac{V_A}{6} + \frac{V_A - V_B}{1}$$

$$\frac{96 - V_A}{4} = \frac{V_A + 6V_A - 6V_B}{6}$$

$$288 - 3V_A = 14V_A - 12V_B$$

$$17V_A - 12V_B = 288 \quad \text{--- (1)}$$

f.t node 3:

By KCL

$$I_3 + 6 = I_4$$

$$\frac{V_A - V_B}{2} + 6 = \frac{V_B}{5}$$

$$\frac{V_A - V_B}{2} - \frac{V_B}{5} = -6$$

$$5V_A - 5V_B - 2V_B = -60$$

$$5V_A - 7V_B = -60 \quad \text{--- (2)}$$

By (1) & (2)

$$\begin{bmatrix} 17 & -12 \\ 5 & -7 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 288 \\ -60 \end{bmatrix}$$

$$\Delta = 17(-7) - 5(-12)$$

$$\therefore \Delta = -59$$

$$\Delta_1 = \begin{vmatrix} 288 & -12 \\ -60 & -7 \end{vmatrix} = -2736$$


$$\Delta_2 = \begin{vmatrix} 17 & 288 \\ 5 & -60 \end{vmatrix} = 17(-60) - 5(288) = -2460$$

$$\therefore V_A = \frac{\Delta_1}{\Delta} = \frac{-2736}{-59} = 46.372 \text{ V}$$

$$V_B = \frac{\Delta_2}{\Delta} = \frac{-2460}{-59} = 41.694 \text{ V}$$

$$\therefore \text{V across } 5\Omega \text{ resistor} = 41.694 \text{ V}$$

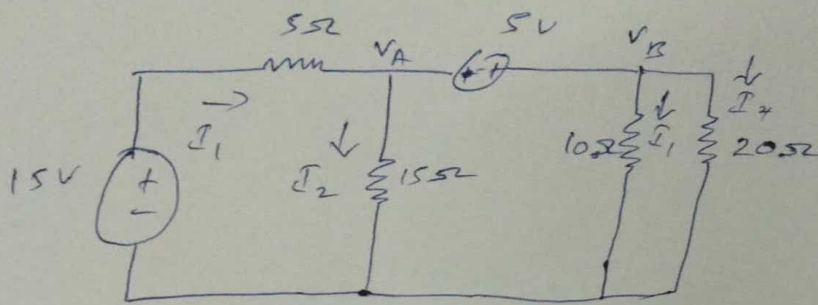4). Using Nodal analysis find voltage across 20Ω resistor in figure



Sol: From diagram using super nodal analysis, we get

$$\boxed{V_A - V_B = 5} \quad \text{--- (1)}$$

At node A

By KCL

$$I_1 = I_2 + I_3 + I_4$$

$$\frac{15 - V_A}{5} = \frac{V_A}{15} + \frac{V_B}{10} + \frac{V_B}{20}$$

$\Rightarrow [\times 5]$

$$15 - V_A = \frac{V_A}{3} + \frac{V_B}{2} + \frac{V_B}{4}$$

$$15 - V_A = \frac{4V_A + 6V_B + 3V_B}{12}$$

$$180 - 12V_A = 4V_A + 9V_B$$

$$\boxed{16V_A + 9V_B = 180} \quad \text{--- (2)}$$

from (1) & (2)

$$\begin{bmatrix} 1 & -1 \\ 16 & 9 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 5 \\ 180 \end{bmatrix}$$

$$\Delta = 9 + 16 = 25$$

$$\Delta_1 = \begin{vmatrix} 5 & -1 \\ 180 & 9 \end{vmatrix} = 45 + 180 = 225$$


$$\Delta_2 = \begin{vmatrix} 1 & 5 \\ 16 & 180 \end{vmatrix} = 180 - 80 = 100$$

$$V_A = \frac{\Delta_1}{\Delta} = 9V$$

$$V_B = \frac{\Delta_2}{\Delta} = 4V$$

\therefore V across 20Ω is $4V$

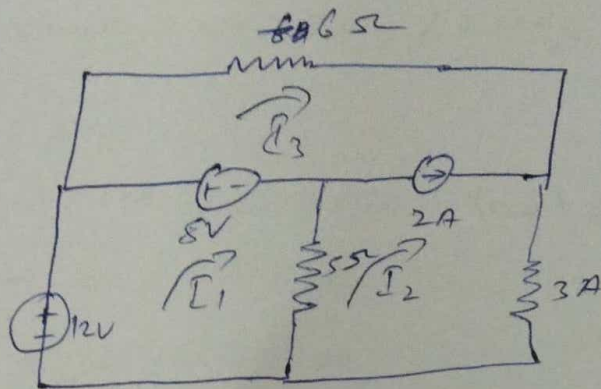Determine the voltage across 3Ω resistor using mesh analysis for the circuit shown in fig.



Sol: From the diagram, applying Super mesh analysis, we get

$$I_2 - I_3 = 2A \quad \text{--- (1)}$$

Loop 1:

$$8 + 5(I_1 - I_2) = 12$$

$$5I_1 - 5I_2 = 4 \quad \text{--- (2)}$$

Loop 2:

loop 2 & loop 3 as single loop \therefore Super Mesh

$$6I_3 + 3I_2 + 5(I_2 - I_1) = 8$$

$$6I_3 + 3I_2 + 5I_2 - 5I_1 = 8$$

$$-5I_1 + 8I_2 + 6I_3 = 8 \quad \text{--- (3)}$$

Solving (2) and (3) get.

$$\begin{bmatrix} 0 & 1 & -1 \\ 5 & -5 & 0 \\ -5 & 8 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 4 \\ 8 \end{bmatrix}$$

$$\Delta = 0 - 1(30 - 0) - 1(40 - 25)$$

$$= -30 - 15$$

$$\Delta = -45$$

$$\Delta_1 = \begin{bmatrix} 2 & 1 & -1 \\ 4 & -5 & 0 \\ 8 & 8 & 6 \end{bmatrix}$$

$$= 2(-30) - 1(24) - 1(32 + 40)$$

$$\therefore \Delta_1 = -156$$

$$\Delta_2 = \begin{vmatrix} 0 & 2 & -1 \\ 5 & 4 & 0 \\ -5 & 8 & 6 \end{vmatrix}$$

$$\Rightarrow 0 - 2(30) - 1(40 + 20)$$


$$\Delta_2 = -120$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-120}{45}$$

$$I_2 = 2.667 \text{ A}$$

$$\therefore V \text{ across } 3\Omega = 2.667 \times 3 = 8 \text{ V}$$

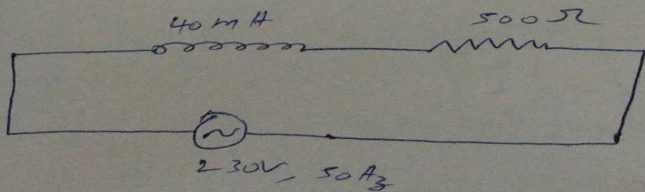- 6). A 500Ω resistor and a 40mH inductor are connected in series across 230V , 50Hz supply. Find circuit impedance, admittance, current, voltage across resistor, voltage across inductor, apparent power, Active power, power factor



$$b = 40 \text{ mH}$$

$$L = 40 \times 10^{-3} \text{ H}$$

$$R = 500 \Omega ; V = 230 \text{ V} ; f = 50 \text{ Hz}$$

$$X_L = L\omega$$

$$= 40 \times 10^{-3} \times 2\pi \times 50$$

$$= 40 \times 10^{-3} \times 314$$

$$\therefore X_L = 12.56 \Omega$$

$$\begin{aligned} \text{(i) Impedance, } Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{(500)^2 + (12.56)^2} \\ Z &= 500.157 \Omega \end{aligned}$$

$$\text{(ii) Admittance} = 1/Z$$

$$Y = 1.99 \times 10^{-3} \Omega^{-1}$$

$$\begin{aligned} \text{(iii) } I_{\text{rms}} &= \frac{V_{\text{rms}}}{Z} \\ &= \frac{230}{500.157} \end{aligned}$$

$$\therefore I_{\text{rms}} = 0.459 \text{ A}$$

$$\begin{aligned} \text{(iv) } V \text{ across } R &= 0.459 \times 500 \\ &= 229.5 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(v) } V \text{ across } L &= 0.459 \times 12.56 \\ &= 5.765 \text{ V} \end{aligned}$$


$$\begin{aligned} \text{(vi) Apparent power} &= VI \\ &= 230 \times 0.459 \\ &= 105.57 \text{ VA} \end{aligned}$$

$$\begin{aligned} \text{(vii) Active power} &= VI \cos \phi \\ &= VI (R/Z) \\ &= 105.57 \times (500/500.157) \\ &= 105.536 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{(viii) Power Factor} &= R/Z \\ (\because \cos \phi &= R/Z) \\ &= 500/500.157 \\ &= 0.999 \\ &\text{No watt} \end{aligned}$$

A series RC circuit with $R = 20\Omega$ and $C = 10\mu F$, $160V, 50Hz$ supply connected to it. Find (i) Impedance (ii) current (iii) power factor (iv) Power. Draw phase Diagram.

Sol.

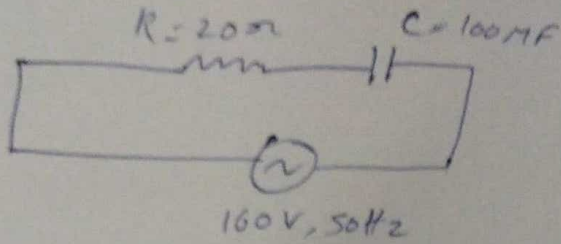

$$R = 20\Omega, C = 100\mu F \quad \therefore V = 160V, f = 50Hz$$

$$= 100 \times 10^{-6} F$$

$$\boxed{C = 10^{-4} F}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{10^{-4} \times 2\pi \times 50}$$

$$= \frac{1}{314 \times 10^{-4}}$$

$$\therefore X_C = 31.847\Omega$$

$$(i) \text{ Impedance, } Z = \sqrt{R^2 + X_C^2} = \sqrt{(20)^2 + (31.847)^2}$$

$$Z = 37.606\Omega$$

$$(ii) \text{ Current, } I = \frac{V}{Z} = \frac{160}{37.606}$$

$$I = 4.254A$$

$$(iii) \text{ Power Factor, } \cos \phi = \frac{R}{Z}$$

$$= \frac{20}{37.606}$$


$$= 0.531$$

$$(iv) \text{ Power} = VI \cos \phi$$


$$= 160 \times 4.254 \times 0.531$$

$$= 361.419W$$

v) Phase Diagram.

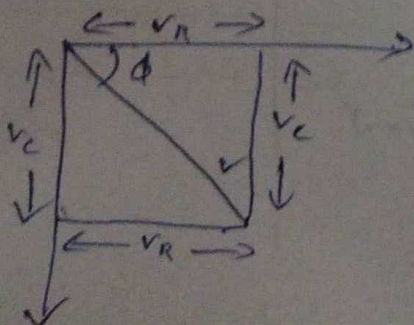

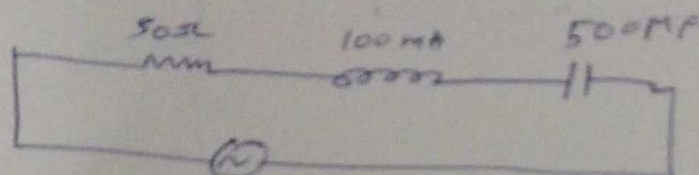In a series RLC circuit $R = 50 \Omega$, $L = 100 \text{ mH}$ and $C = 500 \text{ pF}$ given that the supply voltage is 230 V , 50 Hz . Find equivalent impedance, (ii) power factor, (iii) current, (iv) power and Reactive power.



$$R = 50 \Omega$$

$$L = 100 \text{ mH}$$

$$= 100 \times 10^{-3}$$

$$\therefore L = 10^{-1} \text{ H}$$

$$C = 500 \text{ pF}$$

$$C = 5 \times 10^{-4} \text{ F}$$

$$V = 230 \text{ V}$$

$$f = 50 \text{ Hz}$$

$$X_L = L\omega$$

$$= 10^{-1} \times 2\pi f$$

$$= 31.4 \Omega$$

$$X_C = \frac{1}{L\omega}$$

$$= \frac{1}{5 \times 10^{-4} \times 2\pi f}$$

$$X_C = 6.367 \Omega$$

$$(i) Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{(50)^2 + (31.4 - 6.367)^2}$$

$$Z = 55.915 \Omega$$

$$(ii) \text{ Power factor} = R/Z$$

$$= 0.894$$

$$(iii) I = \frac{V}{Z} \Rightarrow \frac{230}{55.915} \Rightarrow 4.113 \text{ A}$$

$$(iv) \text{ Power} = VI \cos \phi$$

$$= VI (R/Z)$$

$$= 230 \times 4.113 \times 0.894$$

$$= 845.715 \text{ W}$$

$$v) \text{ Reactive power} = VI \sin \phi$$


$$= 230 \times 4.113 \sin (26.619)$$

$$= 422.858 \text{ kV}$$

$$\phi = \cos^{-1} R/Z$$

$$= 26.619$$

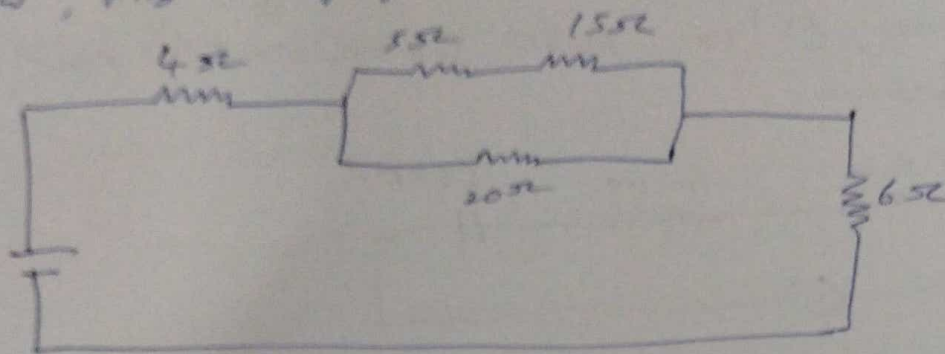- 9) A circuit shown, the power consumed by 6Ω resistor is $150W$, Find the supply voltage.



$P_{6\Omega} = 150W$

$I^2 R = 150$

$I_{6\Omega}^2 = \frac{150}{6}$




$\therefore I_{6\Omega} = 5A$

$R_{eq} = 4 + 6 + 10$

$\therefore R_{eq} = 20\Omega$

$\therefore \text{Supply voltage} = IR \Rightarrow 5 \times 20 \Rightarrow 100V$

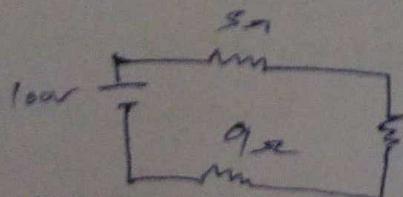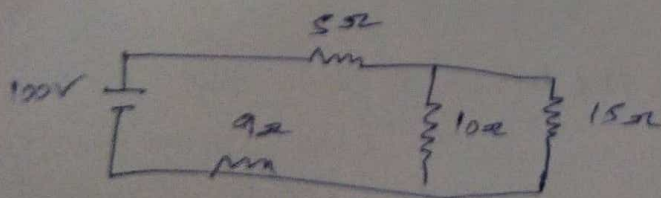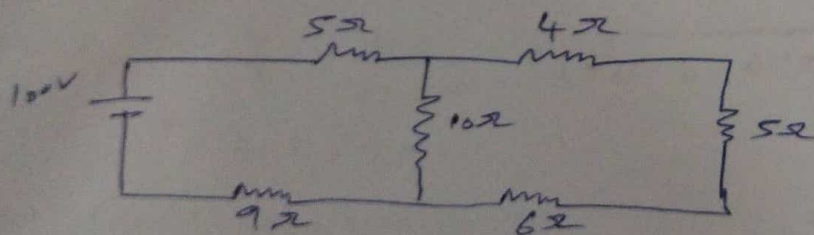- 10). For the circuit shown below, calculate equivalent resistance of the circuit and also the total current.



$\therefore R_{eq} = 20\Omega$

$V = 100V$

$\therefore \text{Total current} = \frac{100}{R} \left(\frac{V}{R} \right)$

$= \frac{100}{20}$

$\therefore \text{Total current} = 5A$
(8)